

Analogue to Digital Conversion II

ENCE361 Embedded Systems 1

Course Coordinator: Ciaran Moore (ciaran.moore@Canterbury.ac.nz)

Lecturer: Le Yang (le.yang@canterbury.ac.nz)


Department of Electrical and Computer Engineering

Where we're going today

- **Uniform quantisation**
- Flash and sigma-delta quantisers
- Dual-slop integrating and successive-approximation quantisers
- ADC in Tiva C-series Launchpad
- Homework

Analogue to Digital Conversion Review

- ADC diagram

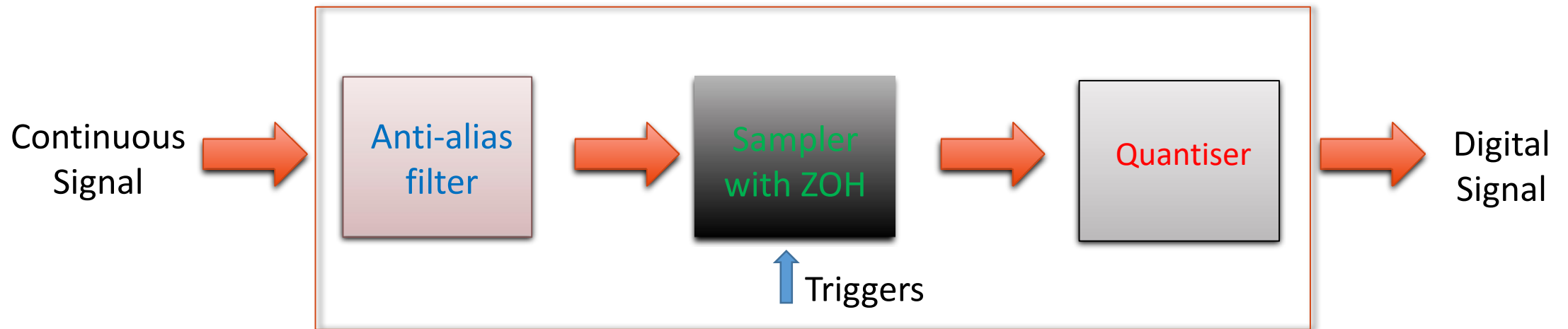


- **Anti-alias filter** removes frequencies of the input that might alias
- **Sampler with zero-order hold (ZOH)** holds the input value until next conversion trigger
- **Quantiser** maps the held input value into **one of possible discrete values**

N-bit Uniform Quantisation

- N-bit uniform quantiser divides voltage range into 2^N equal intervals with **quantization step**

$$\Delta = (V_{\max} - V_{\min}) / 2^N$$

 - For voltage in interval $[k\Delta, (k+1)\Delta]$, $k=0,1,\dots, 2^N-1$, output the binary representation of k
 - Discrete voltage = $(k+(k+1))\Delta/2$
 - Encode** input voltage using N bits
 - Maximum quantisation error amplitude = $\Delta/2$
- Key design question for a uniform quantiser
 - How to determine which quantisation interval the given input belongs to (i.e., how to find k ?)



Quantisation Error

$$N=3 \quad 2^{-4} = \frac{1}{16} \approx 5\% \quad \frac{1}{20} = 5\%$$


- Quantisation error is almost unavoidable in each ADC conversion
- For N-bit uniform quantisation, maximum error amplitude = $\Delta/2$
- Relative maximum amplitude error

$$\frac{\Delta/2}{(V_{max}-V_{min})} = \frac{\left(\frac{V_{max}-V_{min}}{2^N}\right)/2}{(V_{max}-V_{min})} = 2^{-(N+1)}$$

- Quantisation noise power = $\Delta^2/12$
- Exercise: for a sinewave of amplitude A, with N-bit uniform quantisation, what is the signal-to-noise ratio (SNR)? (more in the next lecture)

Where we're going today


$$x \sim U(a, b)$$

 

- Uniform quantization
- **Flash and Sigma-Delta quantisers**
- Dual-slop integrating and successive-approximation quantisers
- ADC in Tiva C-series Launchpad
- Homework



Flash Quantiser

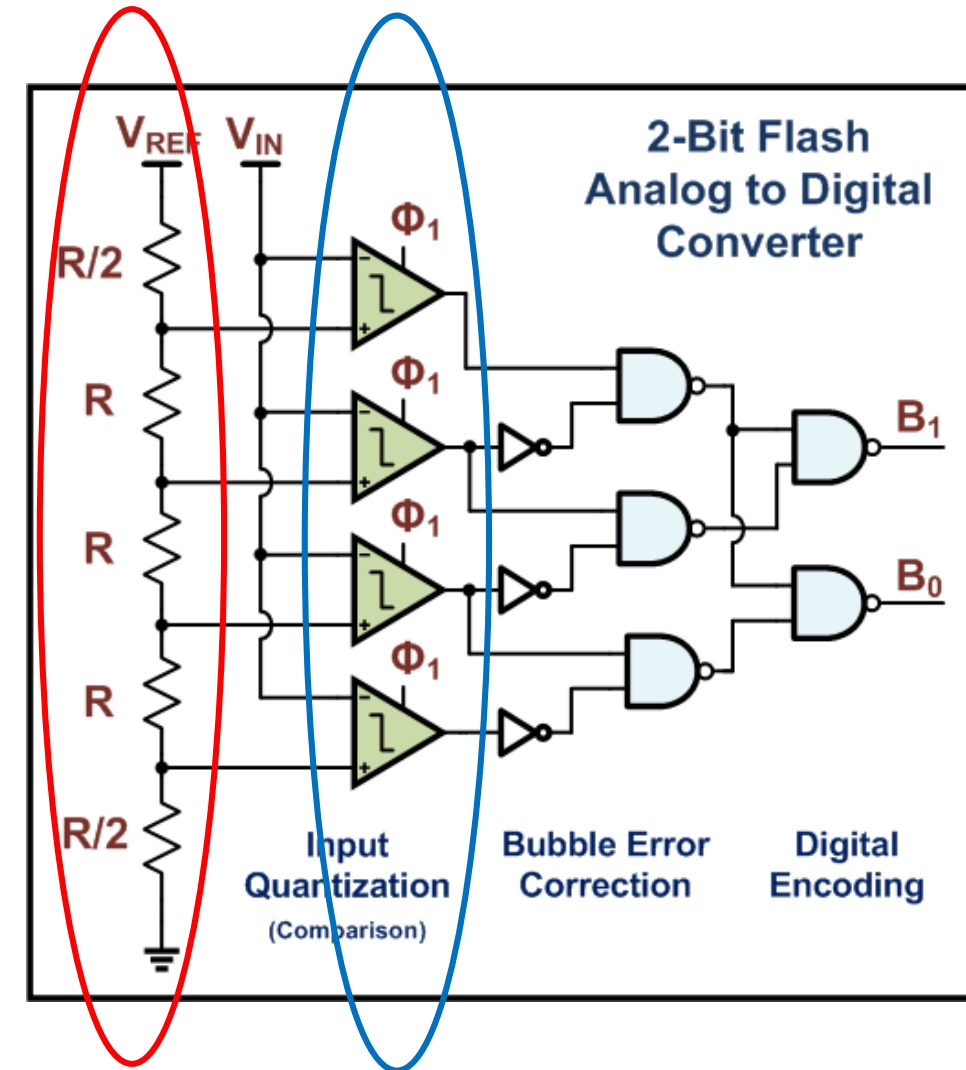- Use voltage ladder to generate successive reference voltages
 - Produce 2^N quantization intervals **simultaneously**
- Use 2^N comparators to find the quantisation interval the input V_{IN} belongs to, **in a single step**
- **Fastest, simple** but could require a huge number of comparators



Sigma-Delta Quantiser

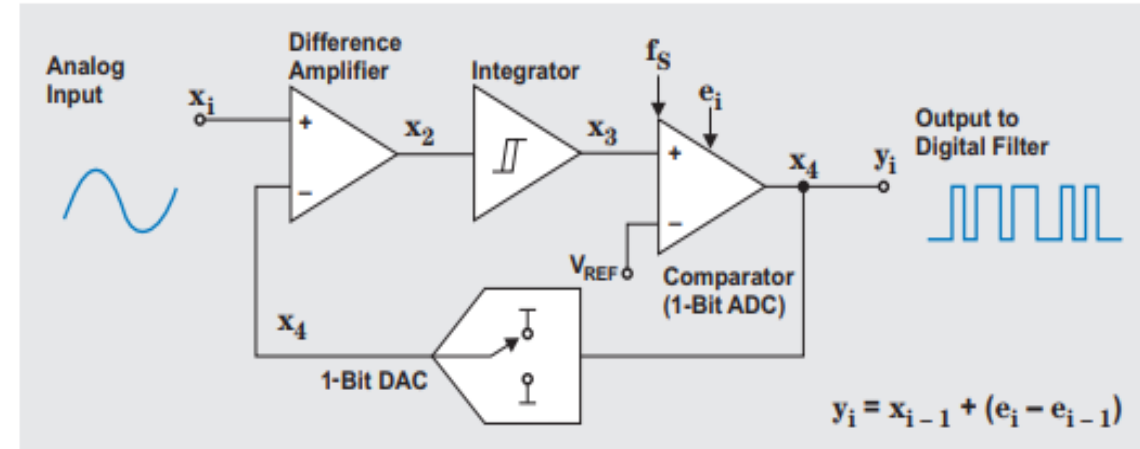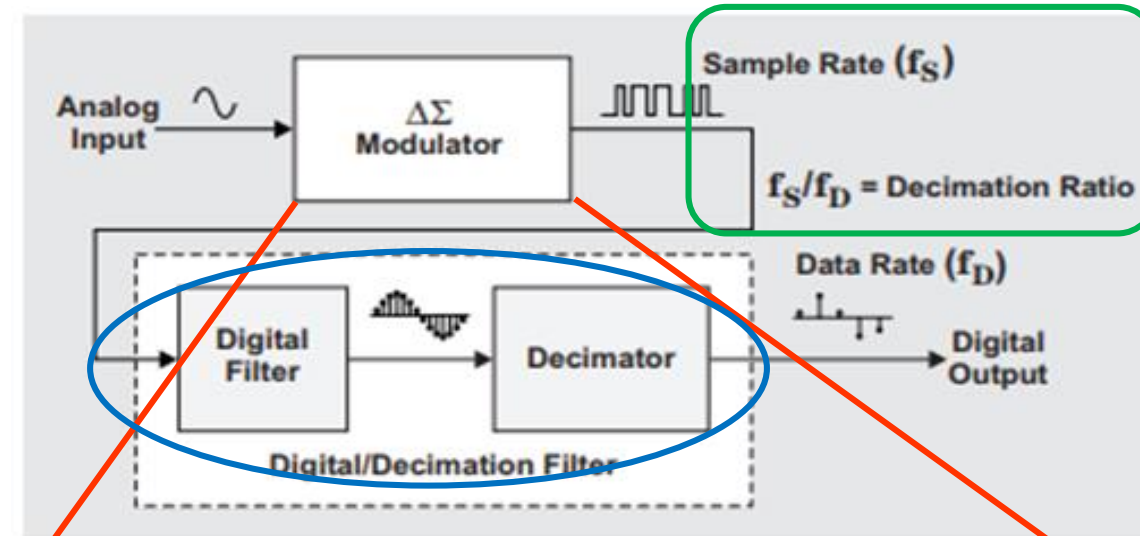- Oversample the analog input
- Sigma-Delta modulator
 - The number of 'ones' in the modulator output is proportional to input value
- Digital/decimator accumulates modulator output over time
 - Output digital signals with required sampling rate
- High resolution, popular in communications engineering



Where we're going today

- Uniform quantization
- Flash and Sigma-Delta quantisers
- **Dual-slop integrating and successive-approximation quantisers**
- ADC in Tiva C-series Launchpad
- Homework

Dual-Slope Integrating Quantiser


- **Phase 1:** reset and charge C using analog input for fixed period T_1
- **Phase 2:** Discharge C using reference input until voltage reaches 0 (say after T_2)

$$V_{IN}T_1 = -V_{REF}T_2$$




$$V_{IN} = -V_{REF}T_2/T_1$$


$$V_{IN} \propto T_2$$

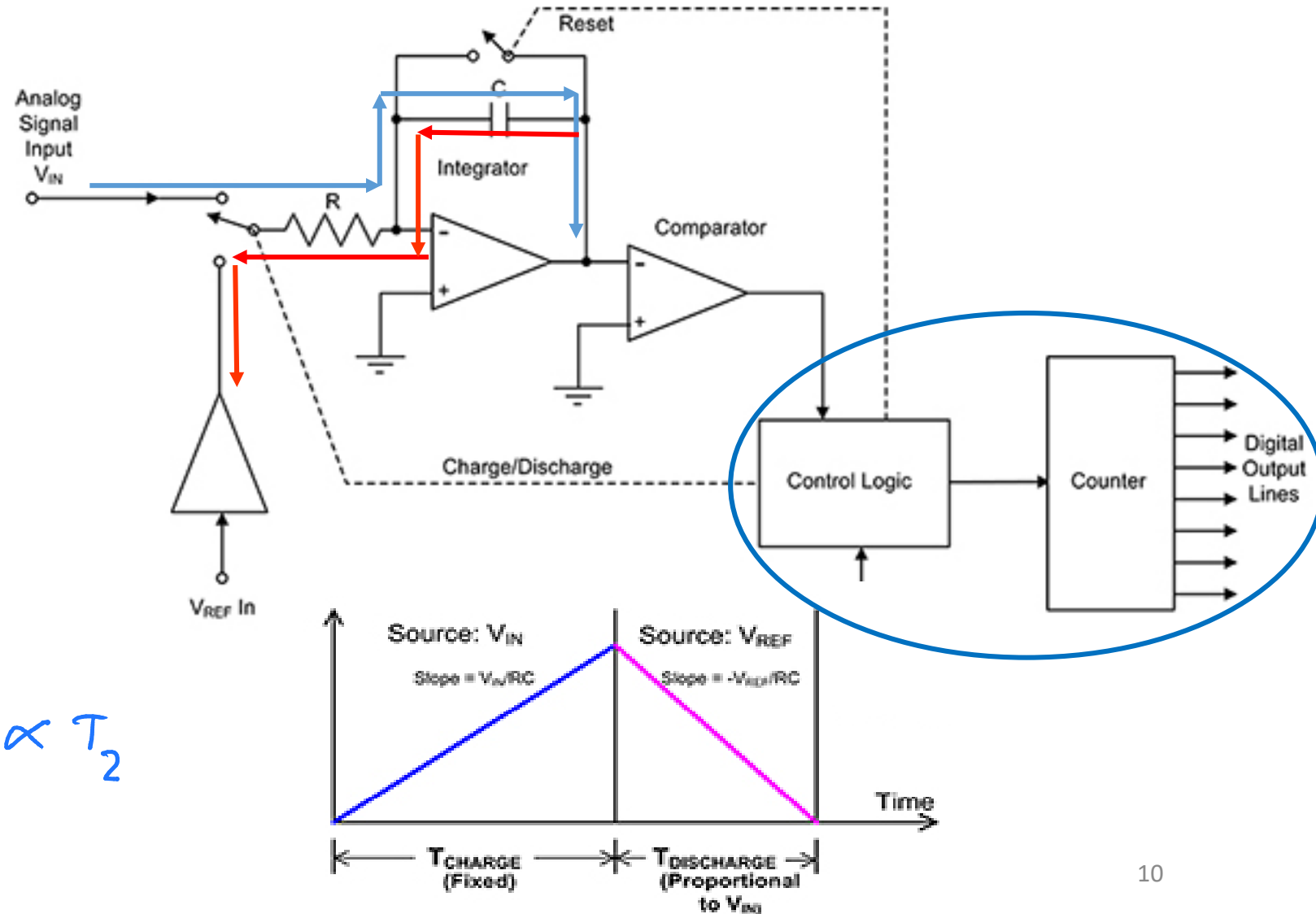

Successive-Approximation Quantiser (1)

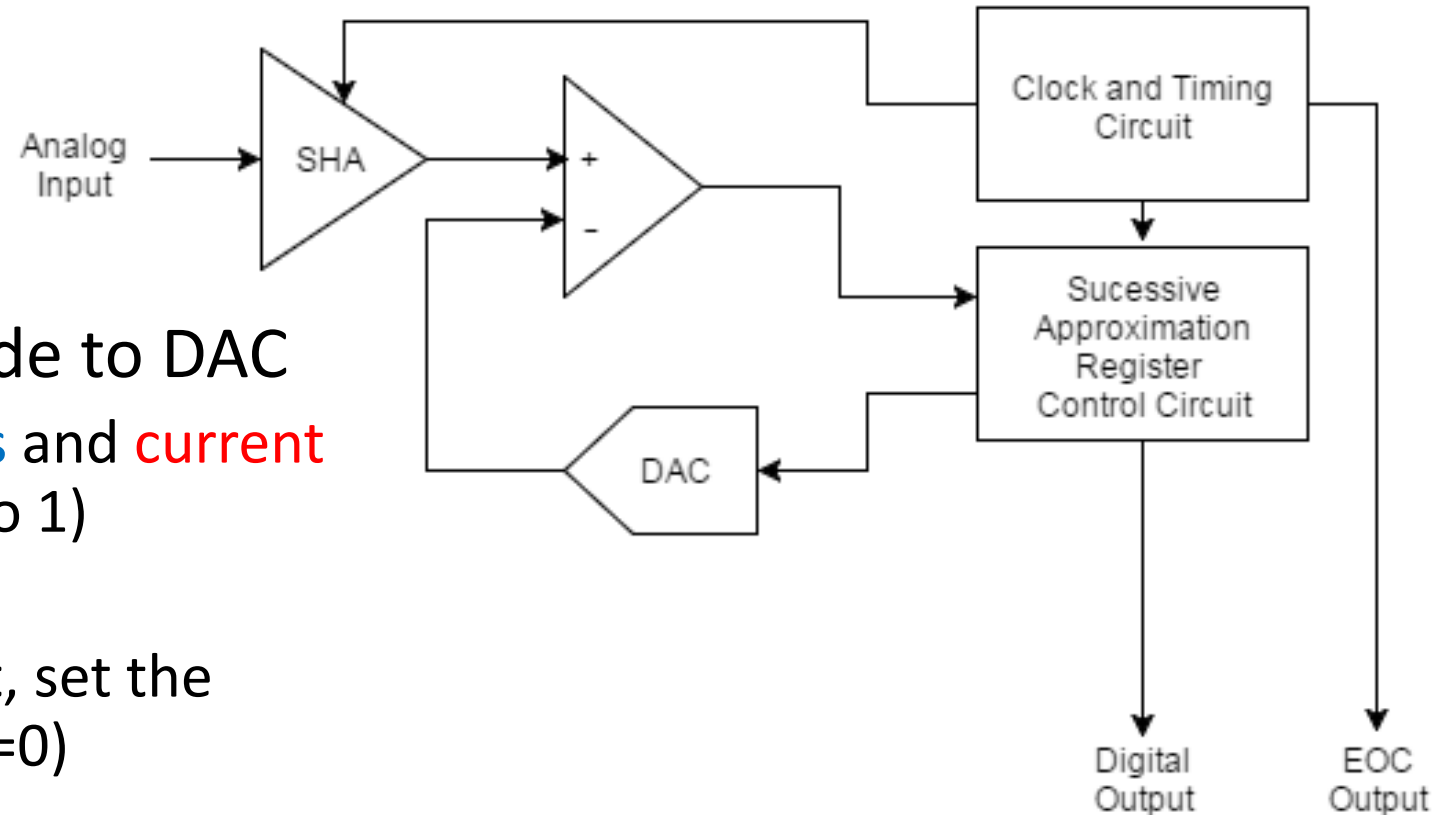- **Hold** the analog input
- Control unit sends binary code to DAC
 - Composed of **determined bits** and **current bit under consideration** (set to 1)
 - DAC produces a value
 - If analog Input \geq DAC output, set the current bit (=1), else clear it (=0)
- Continue until all N bits are determined
 - At least N clock cycles are needed



 

$$N=3$$

$$2^3 = 8$$

↑
8 spaces

Successive-Approximation Quantiser (2)


- Successive-approximation quantisation example
 - 3-bit uniform quantisation with $V_{\max} = 1 \text{ V}$ and $V_{\min} = 0 \text{ V}$, quantization step $\Delta = 1/8$
 - Analogue input = 0.425 V
 - Control unit starts with the binary code **100** $4 \times \frac{1}{8} = 0.5$
 - DAC outputs $0.5 \text{ V} (= 4 \times \Delta) > 0.425 \text{ V} \rightarrow$ the first bit = 0
 - Control unit proceeds with the binary code **010** $2 \times \frac{1}{8} = \frac{1}{4} = 0.25$
 - DAC outputs $0.25 \text{ V} (= 2 \times \Delta) < 0.425 \text{ V} \rightarrow$ the second bit = 1
 - Control unit proceeds with the binary code **011** $3 \times \frac{1}{8} = \frac{3}{8}$
 - DAC outputs $0.375 \text{ V} (= 3 \times \Delta) < 0.425 \text{ V} \rightarrow$ the third bit = 1
 - Control unit outputs with the quantisation result **011**

Where we're going today

- Uniform quantization
- Flash and Sigma-Delta quantisers
- Dual-slop integrating and successive-approximation quantisers
- **ADC in Tiva C-series Launchpad**
- Homework


12-bit ADC Module (1)

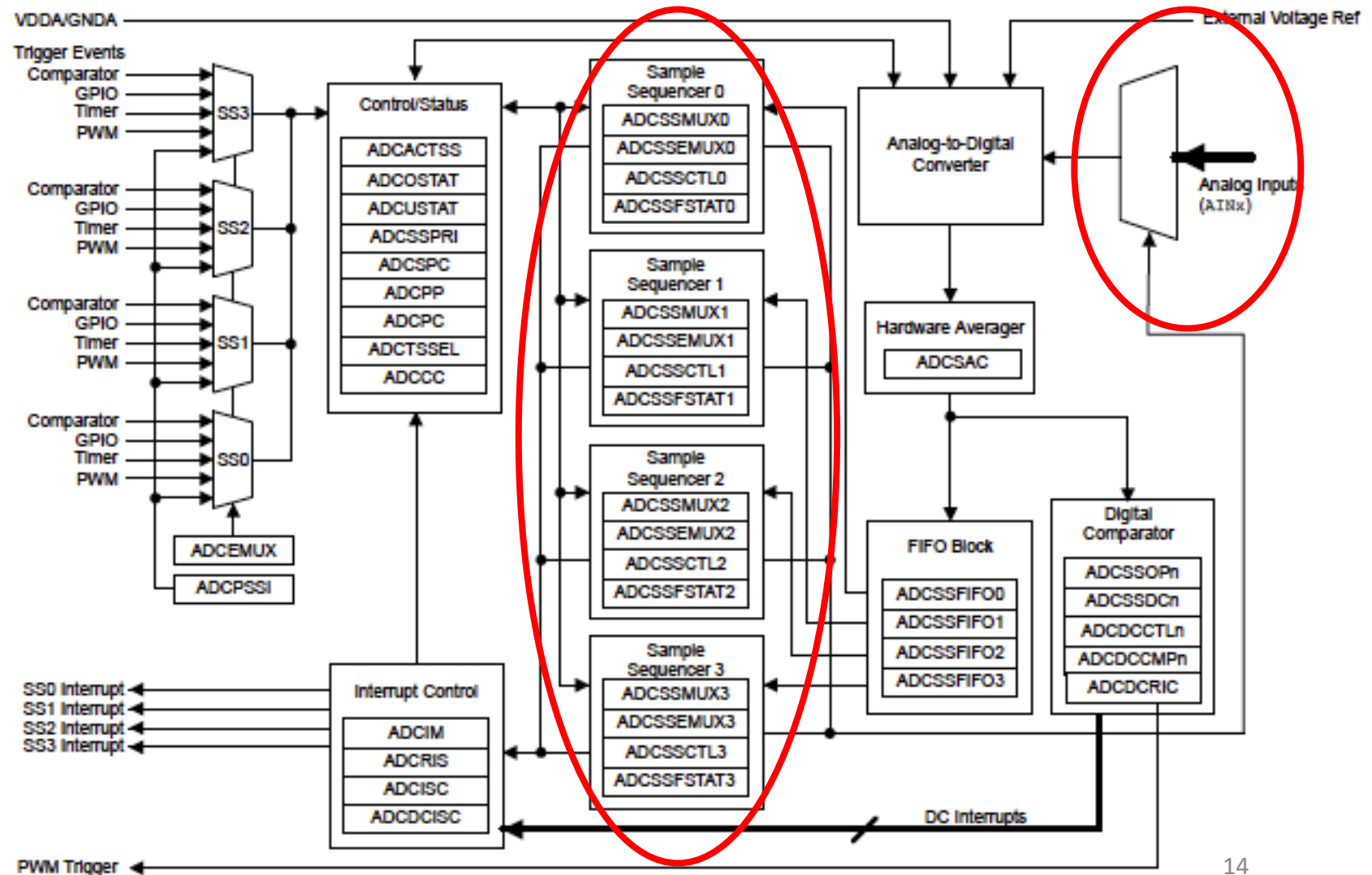- 2 ADC modules
 - 4 sample sequencers in each module
 - Each sequencer with **configurable** trigger
 - Each sequencer has 1, 4 or 8 steps
- Tiva C-series Launchpad ADC supports 8 input channels and an **internal** temperature sensor




12-bit ADC Module (2)

Sample sequencer structure

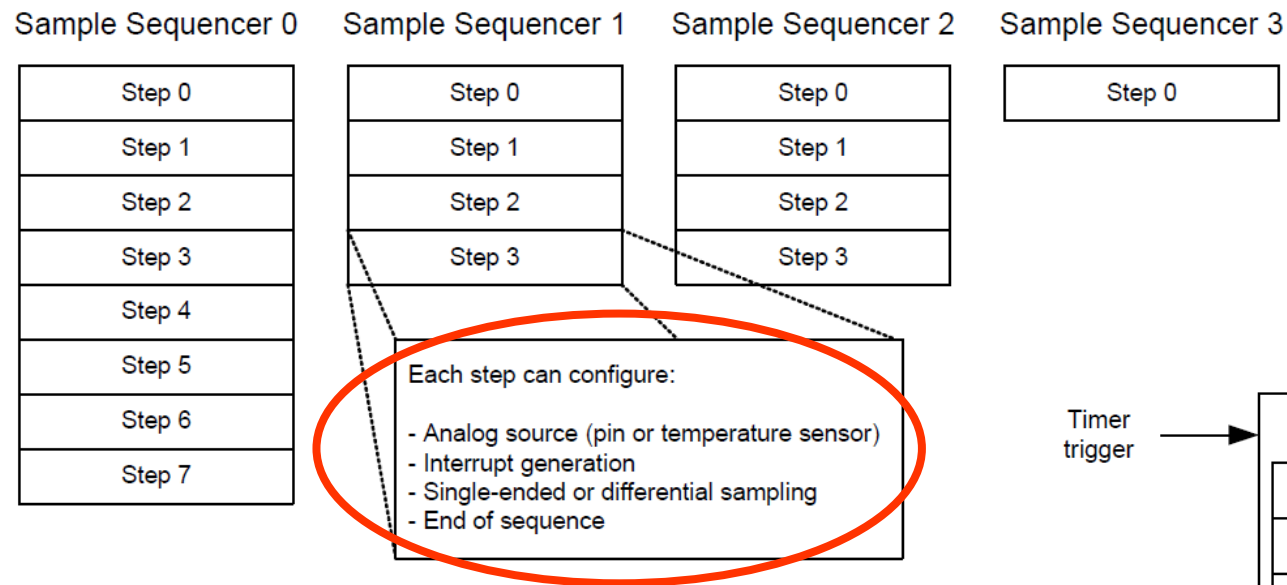

Example system configuration

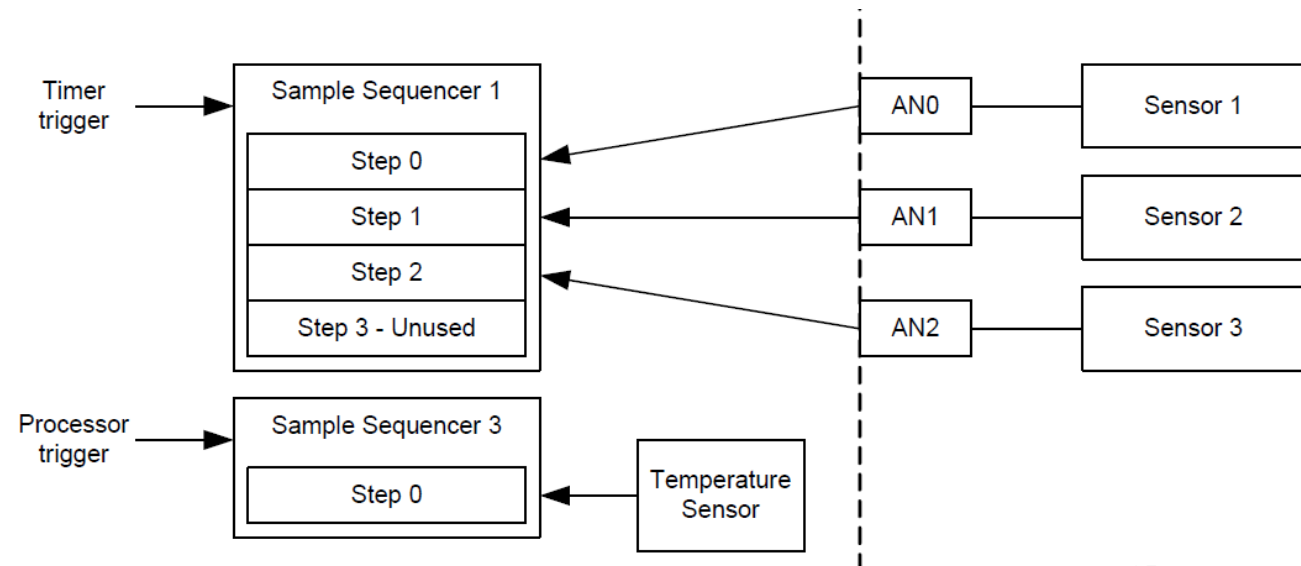

Example Code for ADC Initialization

```
void initADC (void)
{
    // Enable ADC0 module for configuration and use
    SysCtlPeripheralEnable(SYSCTL_PERIPH_ADC0);

    // Enable sample sequencer 3 with a processor signal trigger (ADC_TRIGGER_PROCESSOR)
    ADCSequenceConfigure(ADC0_BASE, 3, ADC_TRIGGER_PROCESSOR, 0);

    // Configure step 0 on sequencer 3
    // Sample channel 0 (ADC_CTL_CH0) is single-ended mode (default)
    // Configure the interrupt flag (ADC_CTL_IE) to be set when the sample is done
    // Tell the ADC logic that this is the last conversion on sequence 3 (ADC_CTL_END)
    ADCSequenceStepConfigure(ADC0_BASE, 3, 0, ADC_CTL_CH0 | ADC_CTL_IE | ADC_CTL_END);

    // Enable Sequencer 3 in ADC0
    ADCSequenceEnable(ADC0_BASE, 3);

    .
    .
}
```

Homework


1. Understand the example code `ADCdemo1.c` with help of the following documents
 - Using the Stellaris Microcontroller Analog-to-Digital Converter (ADC).pdf
 - TivaWare Peripheral Driver Library Users Manual.pdf
2. What type of ADC is used on the Tiva C-Series Launchpad?
3. What common instrument uses a dual-slope integrating ADC?
4. How many analog channels are supported by the Tiva C-Series Launchpad ADC?
5. What is the range of quantisation error in volts for an 8-bit quantiser with an input range 0 – 3 V? Repeat for 10-bit and 12-bit ADCs.
6. If the maximum signal frequency is 500 Hz and 12-bit quantization is being performed with signal averaging over 15 consecutive samples, what is the minimum sampling rate?

Digital to Analogue Conversion (DAC)

- Digital input controls switches
- Operational amplifier sums up the currents and converts to voltage for output

$$V_{out} = -V_{cc} \sum_{i=0}^3 \frac{R_1}{2^{3-i}R} b_i$$

- DAC accuracy relies on resistances

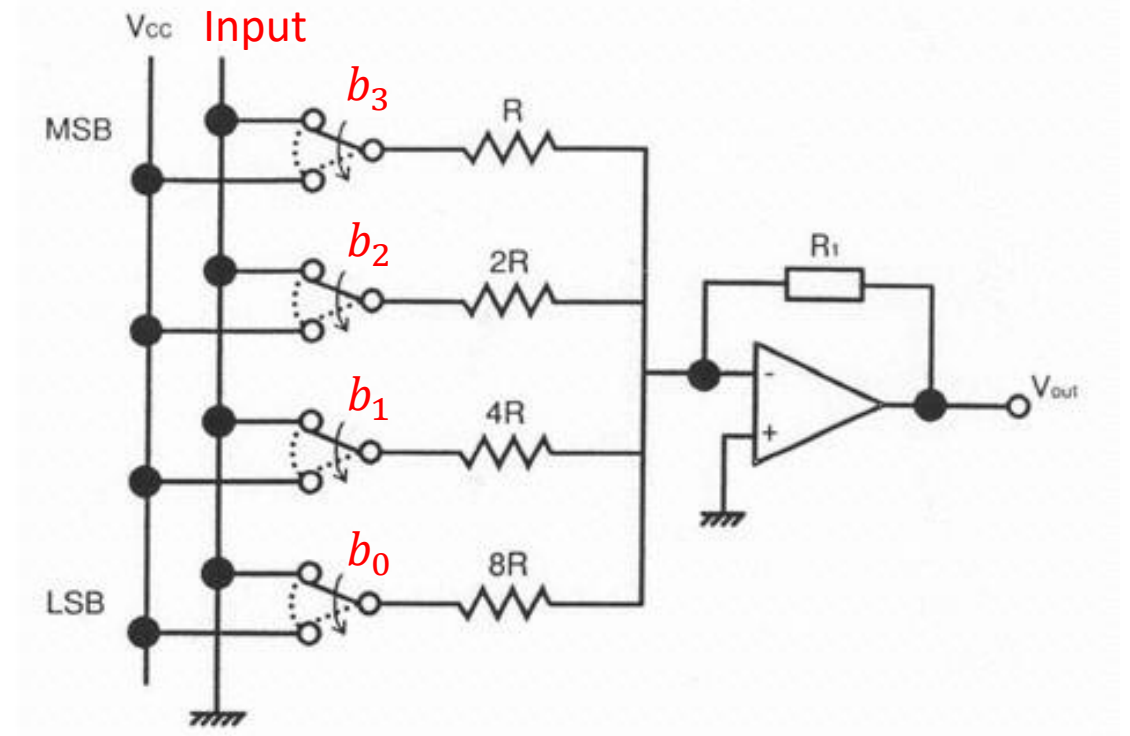

4-bit DAC