

Debouncing

ENCE361 Embedded Systems 1

Course Coordinator: Ciaran Moore (ciaran.moore@Canterbury.ac.nz)

Lecturer: Le Yang (le.yang@canterbury.ac.nz)

Department of Electrical and Computer Engineering


Where we're going today

- **Switch bounce**
- Hardware debouncing
- Software debouncing
- Homework

Switch Bounce (1)


- After pushing a button (closing switch), two metal parts **repeat connecting and separating multiple times** over a short interval before settling down

Simple pull-up switch

 


- Switch bounce could also occur when releasing a switch

V_{out} on an oscilloscope

 

Switch Bounce (2)

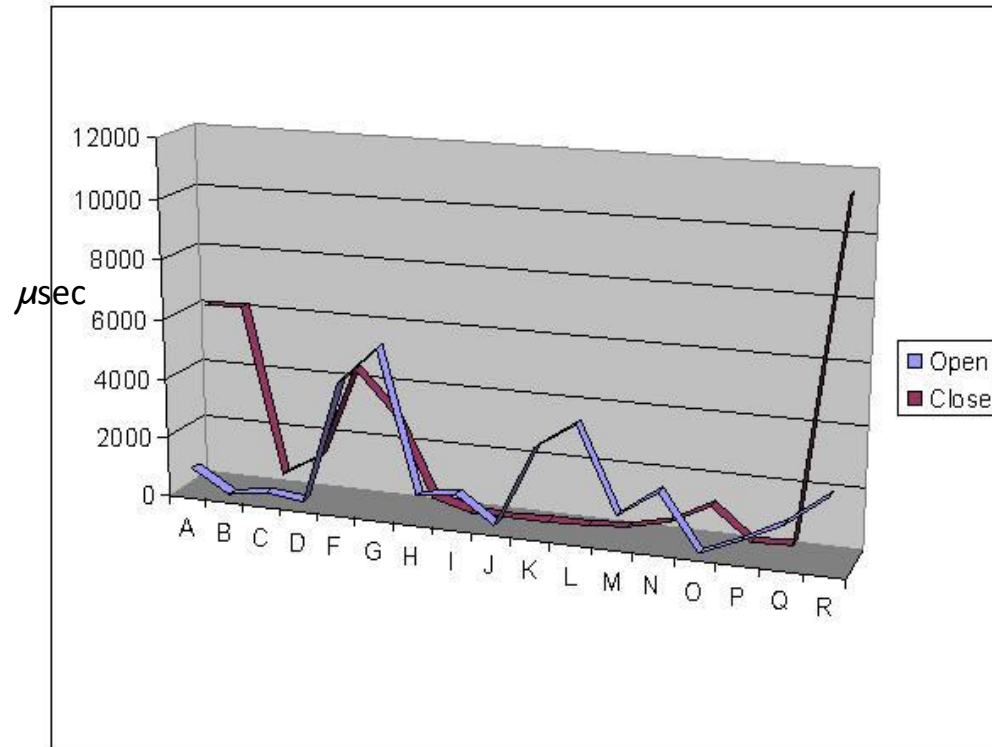- Have to live with (somewhat) **unpredictable switch bounce behaviour**




*Bounce times in microseconds, for opening and closing each switch (number A to R).
Switch E was left out, as its 157 msec bounces would horribly skew the graph.*

- Bounce times in μsec when pushing and releasing 20 switches
- Switch E was left out due to its 157 msec bounce time (around 1/6 second!)

Switch Bounce (3)

 - Switch bounce in TV remote control ...
 - How many times was the button pushed?



Analogue Output



Digital Output

Where we're going today

- Switch bounce
- **Hardware debouncing**
- Software debouncing
- Homework

Debouncer for Double-Throw Switch (1)

  - Debouncing: processing switch signal so that a single press would not be interpreted as multiple presses
- Double-throw switch debouncing using a SR flip-flop




Double-throw switch
sold on Amazon

The press is **locked**
once detected

Debouncer for Double-Throw Switch (2)

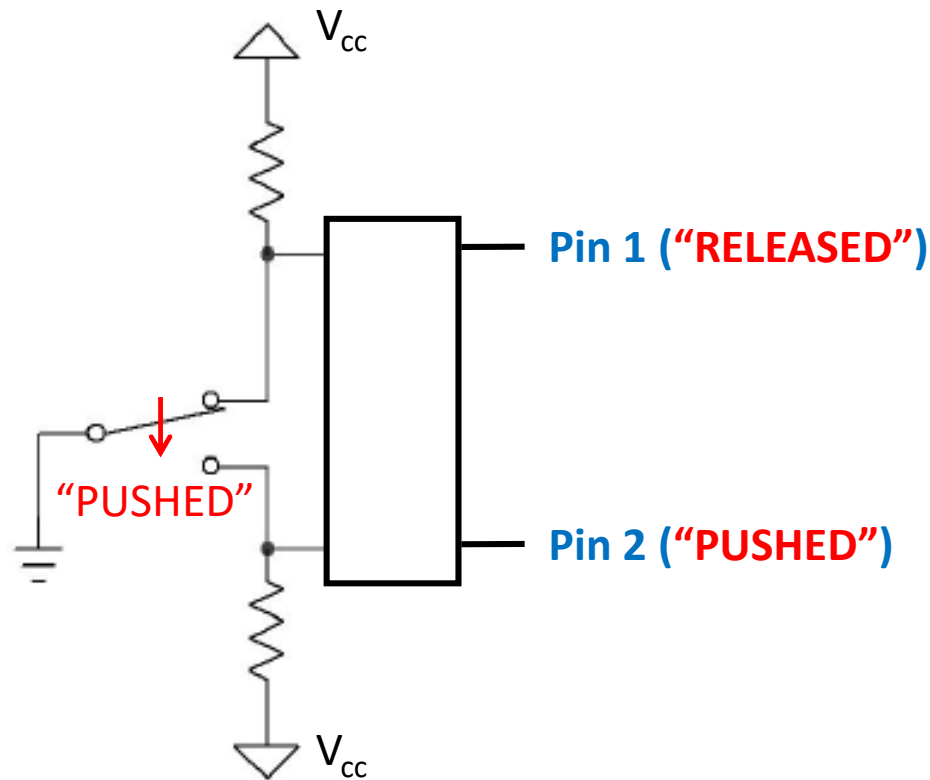- Conceptually, SR-based double-throw switch debouncer is equivalent to





Software version of the debounced double-throw switch

```
if (pin2()) // Detect "PUSH" operation
    state = PUSHED;
```

```
if (!pin1()) // Detect "RELEASE" operation
    state = RELEASED;
```


RC Circuit-based Debouncer

  - Double-throw switch is bulky and single-throw switches are more common
- Debouncing using RC circuit and Schmitt trigger




Where we're going today

- Switch bounce
- Hardware debouncing
- **Software debouncing**
- Homework

Switches on Tiva C-Series Launchpad

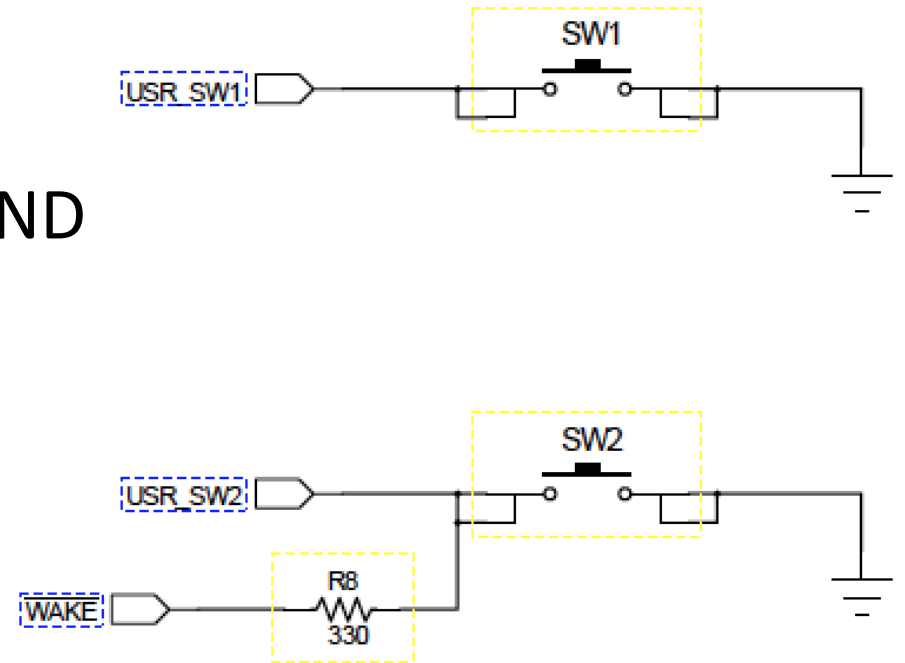- Two single-throw switches: SW1 and SW2
- Pushing a button connects a GPIO pin to GND
 - SW1 → PF4
 - SW2 → PF0
- **No debouncing circuitry**
 - Software debouncing is a must



Software Debouncing (1)

- Basic idea
 - Switch bounce causes multiple contacting-separation cycles over a short period
 - Voltage settles down after switch bounce
 - **N consecutive readings that are the same**
 - Indicating that pushing/releasing a button has been completed *reliably*
- How to poll the pin to obtain voltage readings?
 - Pin-change interrupt-based polling
 - Many rapid voltage changes → many interrupts causing MCU to be fully occupied for several ms
 - Regular polling using timers (e.g., SysTick at 100 Hz)
 - Still an interrupt-based approach but with better MCU scheduling

Software Debouncing (2)

- Algorithm
 - Suppose switch button stays at **RELEASED**
 - Poll the pin connecting the switch at a fixed rate
 - If pin read is **PUSHED**
 - If pin read has been **PUSHED** for N_1 consecutive reads
 - Change the button state to **PUSHED**
 - If pin read is **RELEASED**
 - Stay at **RELEASED**

Sounds complicated? 😊

Finite State Machine (FSM)


- In computer science, finite state automaton (FSA)

- State

- **PUSHED** and **RELEASED**

- Triggers-based state transition

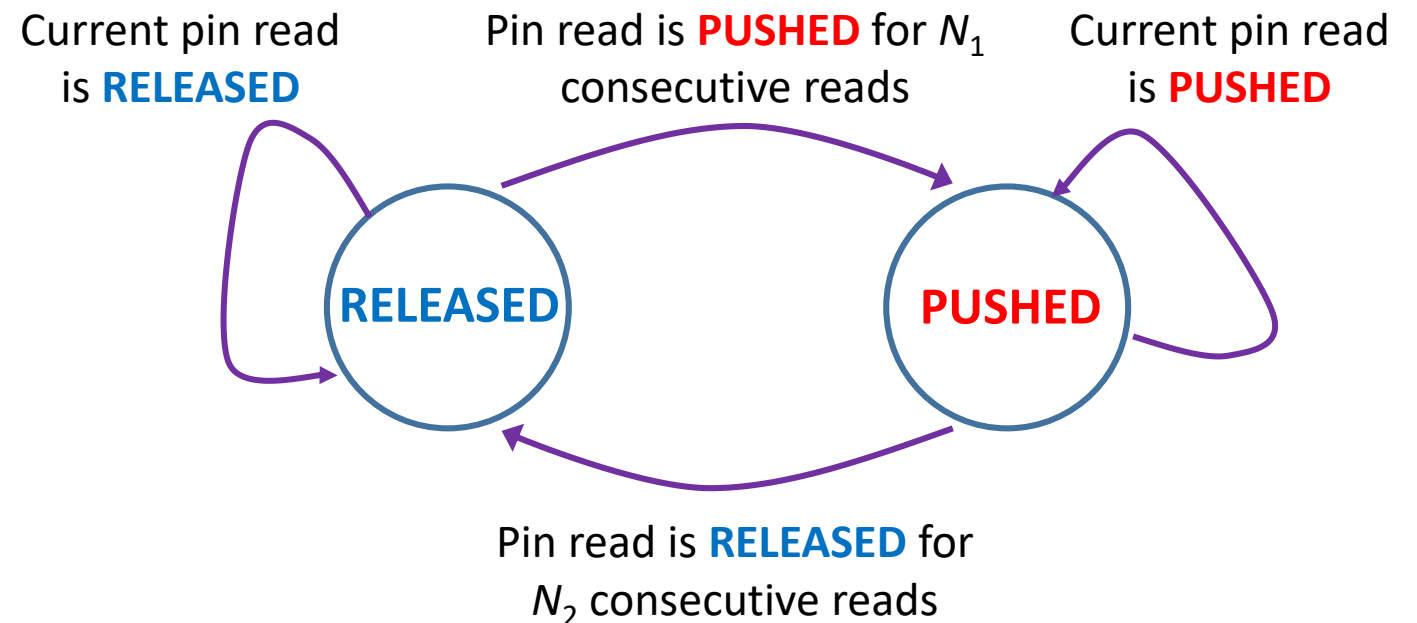- **RELEASED** → **PUSHED**
 - **RELEASED** → **RELEASED**
 - **PUSHED** → **RELEASED**
 - **PUSHED** → **PUSHED**



Design Considerations

- Choose **a relatively low value for N_1** for a rapid response to pushing button
- Select **a relatively large value for N_2** to reduce false detections
- Multiple buttons can be polled when servicing each (say SysTick) interrupt
- A state variable that takes the value of **PUSHED** or **RELEASED** can be maintained for each button

Example Code: **buttons4.h**

```
// buttons4.h
```

```
// Support for a set of four specific buttons on the Tiva/Orbit
```

```
// The buttons are: UP and DOWN (on Orbit daughterboard) + RIGHT & LEFT on Tiva board
```

```
enum butNames {UP = 0, DOWN, LEFT, RIGHT, NUM_BUTS};
```

```
enum butStates {RELEASED = 0, PUSHED, NO_CHANGE};
```

```
// UP button
```

```
#define UP_BUT_PERIPH  SYSCTL_PERIPH_GPIOE
```

```
#define UP_BUT_PORT_BASE  GPIO_PORTE_BASE
```

```
#define UP_BUT_PIN  GPIO_PIN_0
```

```
#define UP_BUT_NORMAL  false
```

```
// DOWN button
```

```
#define DOWN_BUT_PERIPH  SYSCTL_PERIPH_GPIOD
```

```
#define DOWN_BUT_PORT_BASE  GPIO_PORTD_BASE
```

```
#define DOWN_BUT_PIN  GPIO_PIN_2
```

```
#define DOWN_BUT_NORMAL  false
```


Example Code: buttons4.c

```
static bool but_state[NUM_BUTS];           // State variables (PUSHED/RELEASED) for 4 buttons
static uint8_t but_count[NUM_BUTS];

void updateButtons (void) {
    bool but_value[NUM_BUTS];
    int i;
    // Poll UP and DOWN buttons
    but_value[UP] = (GPIOPinRead (UP_BUT_PORT_BASE, UP_BUT_PIN) == UP_BUT_PIN);
    but_value[DOWN] = (GPIOPinRead (DOWN_BUT_PORT_BASE, DOWN_BUT_PIN) == DOWN_BUT_PIN);
    for (i = 0; i < NUM_BUTS; i++) {
        if (but_value[i] != but_state[i]) {
            but_count[i]++;                // Record current pin read if it is different from the pin state
            if (but_count[i] >= NUM_BUT_POLLS) { // State transition for button i
                but_state[i] = but_value[i];
                but_count[i] = 0;
            }
        }
        else
            but_count[i] = 0;              // Stay in the pin state
    }
}
```

Homework

1. With reference to Slide 9, explain how the RC debouncer works and the role of the Schmitt trigger. What is a disadvantage of this hardware method of debouncing?
2. Why are pin-change interrupts for debouncing button pushes **not** recommended?
3. Why are timer generated interrupts recommended for button polling (Slide 12)?
4. Write a modified version of **updateButtons()** which implements the dual count (N_1 , N_2) algorithm described on Slide 14.